
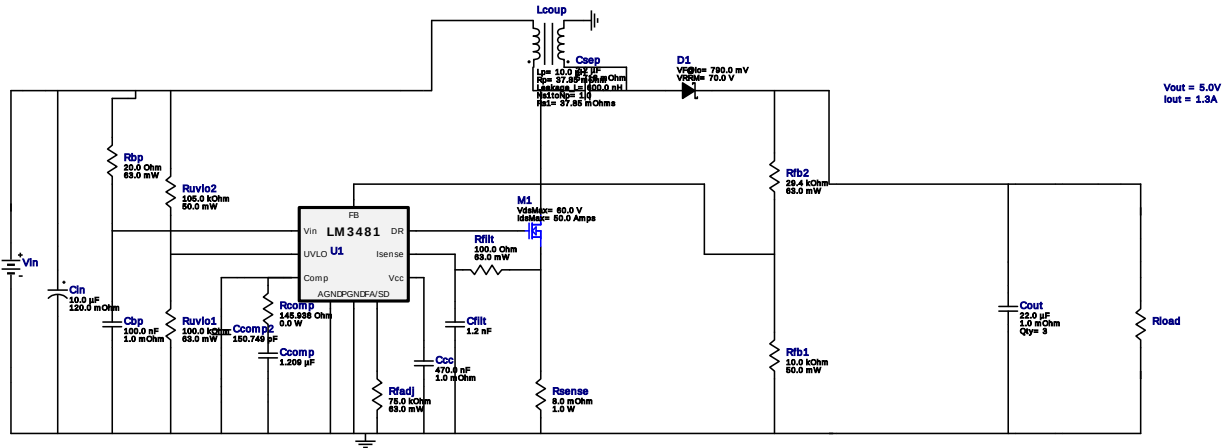



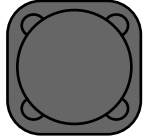








1. Please note that Loop/ stability model has not been implemented for this device. The operating values and charts related to loop model are disabled.

Electrical BOM


Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
Cbp	TDK	C2012X7T2E104K125AA Series= X7T	Cap= 100.0 nF ESR= 1.0 mOhm VDC= 250.0 V IRMS= 0.0 A	1	\$0.09	 0805 7 mm ²
Ccc	MuRata	GRM155R61A474KE15D Series= X5R	Cap= 470.0 nF ESR= 1.0 mOhm VDC= 10.0 V IRMS= 0.0 A	1	\$0.02	 0402 3 mm ²
Ccomp	CUSTOM	CUSTOM Series= ?	Cap= 1.209 uF VDC= 0.0 V IRMS= 0.0 A	1	NA	CUSTOM 0 mm ²
Ccomp2	CUSTOM	CUSTOM Series= ?	Cap= 150.749 pF VDC= 0.0 V IRMS= 0.0 A	1	NA	CUSTOM 0 mm ²
Cfilt	TDK	C2012C0G1H122J060AA Series= C0G/NP0	Cap= 1.2 nF VDC= 50.0 V IRMS= 0.0 A	1	\$0.02	 0805 7 mm ²
Cin	Panasonic	EEHZA1J100P Series= ZA	Cap= 10.0 uF ESR= 120.0 mOhm VDC= 63.0 V IRMS= 1.0 A	1	\$0.66	 SM_RADIAL_6.3AMM 80 mm ²
Cout	Taiyo Yuden	LMK212BJ226MG-T Series= X5R	Cap= 22.0 uF ESR= 1.0 mOhm VDC= 10.0 V IRMS= 1.6 A	3	\$0.09	 0805 7 mm ²
Csep	TDK	C3216X7S2A225K160AB Series= X7S	Cap= 2.2 uF ESR= 5.718 mOhm VDC= 100.0 V IRMS= 3.03632 A	1	\$0.18	 1206_180 11 mm ²

Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
D1	Diodes Inc.	B370-13-F	VF@Io= 790.0 mV VRRM= 70.0 V	1	\$0.24	 SMC 83 mm ²
Lcoup	Coiltronics	DRQ125-100-R	Lp= 10.0 µH Rp= 37.85 mOhm Leakage_L= 600.0 nH Ns1toNp= 1.0 Rs1= 37.85 mOhms	1	\$0.79	 DRQ125 210 mm ²
M1	Texas Instruments	CSD18534Q5A	VdsMax= 60.0 V IdsMax= 50.0 Amps	1	\$0.42	 DQJ0008A 55 mm ²
Rbp	Vishay-Dale	CRCW040220R0FKED Series= CRCW..e3	Res= 20.0 Ohm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
Rcomp	CUSTOM	CUSTOM Series= ?	Res= 145.938 Ohm Power= 0.0 W Tolerance= 0.0%	1	NA	CUSTOM 0 mm ²
Rfadj	Vishay-Dale	CRCW040275K0FKED Series= CRCW..e3	Res= 75.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
Rfb1	Yageo	RC0201FR-0710KL Series= ?	Res= 10.0 kOhm Power= 50.0 mW Tolerance= 1.0%	1	\$0.01	 0201 2 mm ²
Rfb2	Vishay-Dale	CRCW040229K4FKED Series= CRCW..e3	Res= 29.4 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
Rfilt	Vishay-Dale	CRCW0402100RFKED Series= CRCW..e3	Res= 100.0 Ohm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
Rsense	Susumu Co Ltd	PRL1632-R008-F-T1 Series= PRL1632	Res= 8.0 mOhm Power= 1.0 W Tolerance= 1.0%	1	\$0.20	 0612 11 mm ²
Ruvlo1	Vishay-Dale	CRCW0402100KFKED Series= CRCW..e3	Res= 100.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
Ruvlo2	Yageo	RC0201FR-07105KL Series= ?	Res= 105.0 kOhm Power= 50.0 mW Tolerance= 1.0%	1	\$0.01	 0201 2 mm ²
U1	Texas Instruments	LM3481MM/NOPB	Switcher	1	\$1.24	DGS0010A_N 24 mm ²

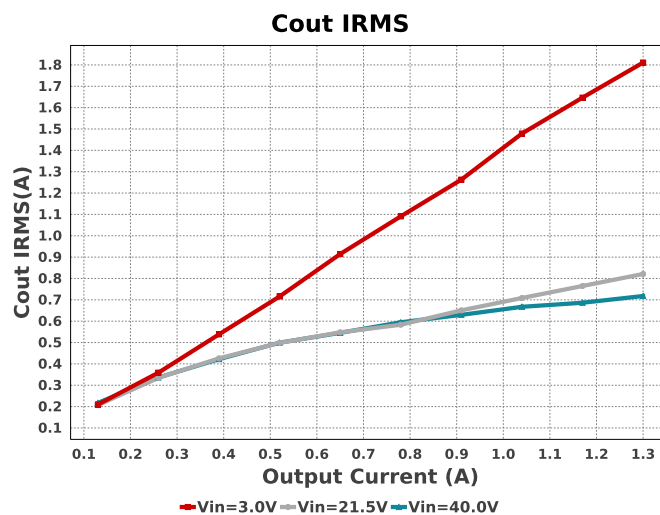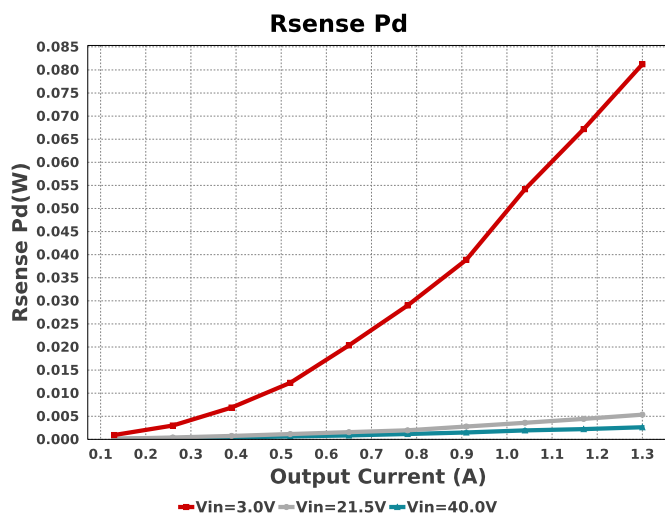


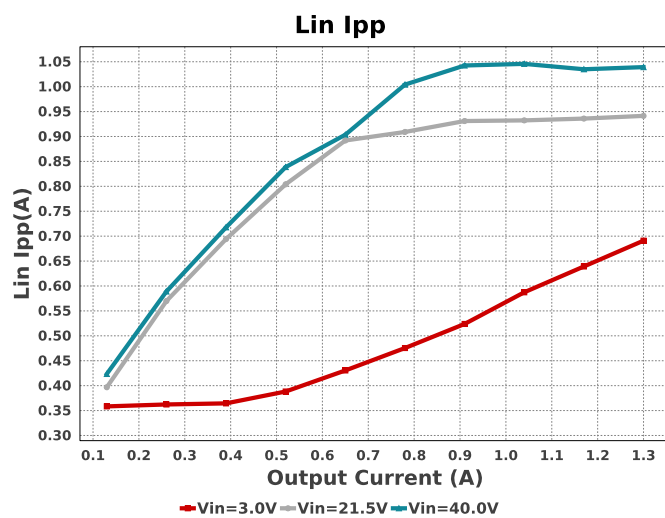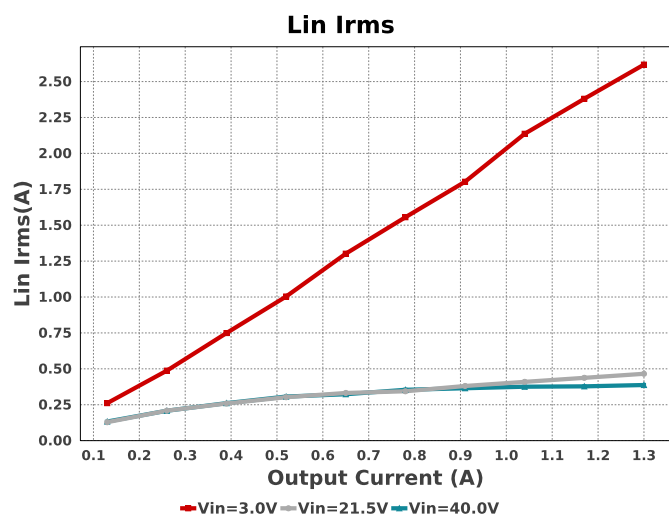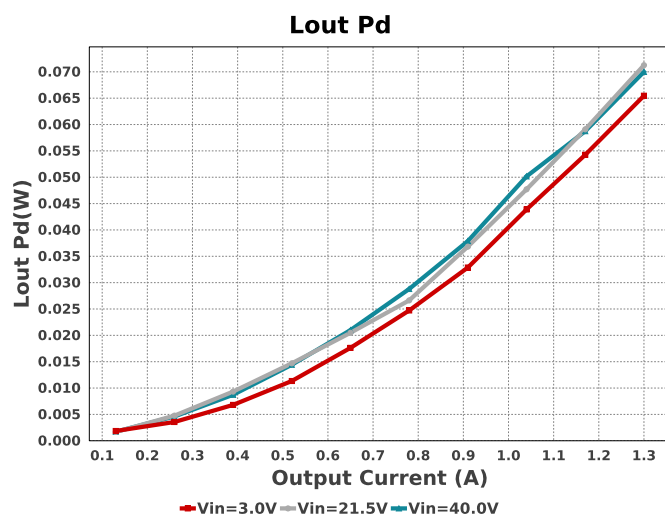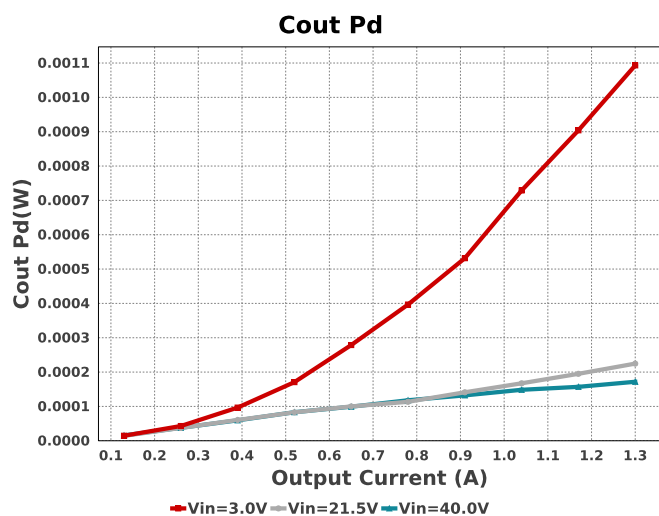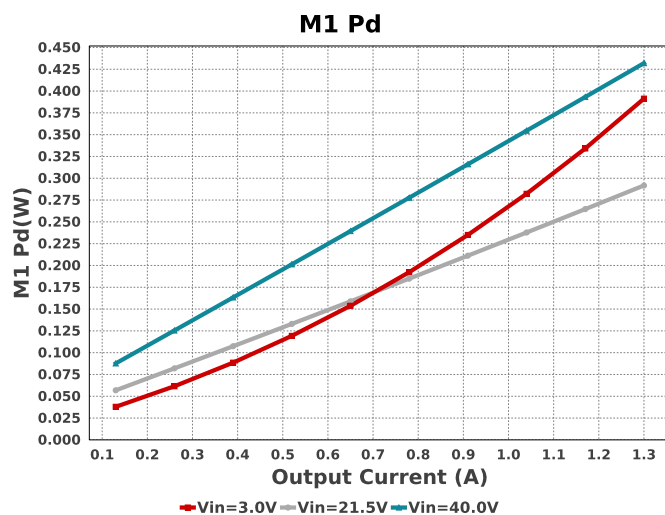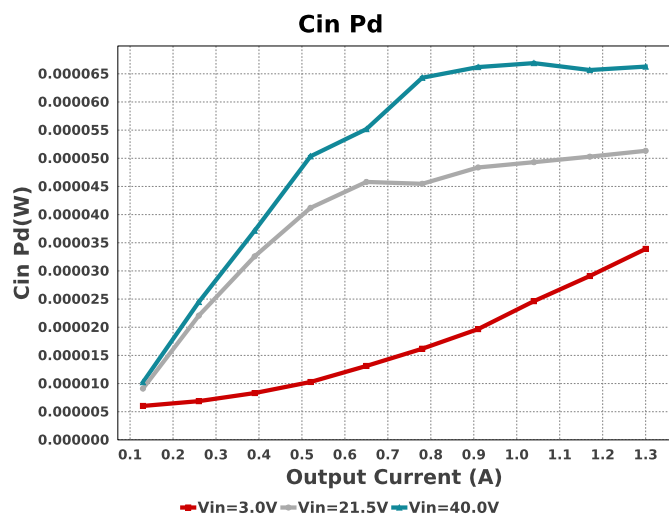


Lin Ipk

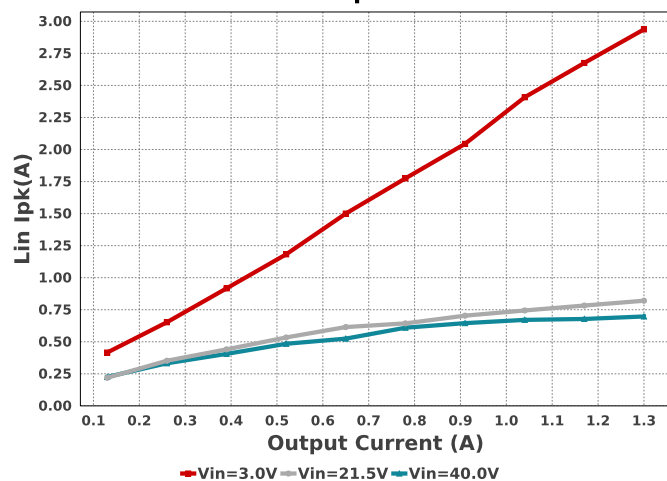


D1 Tj

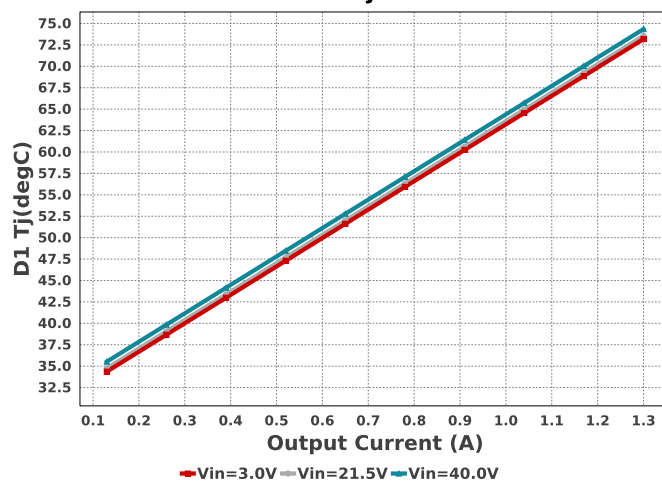


Iin Avg

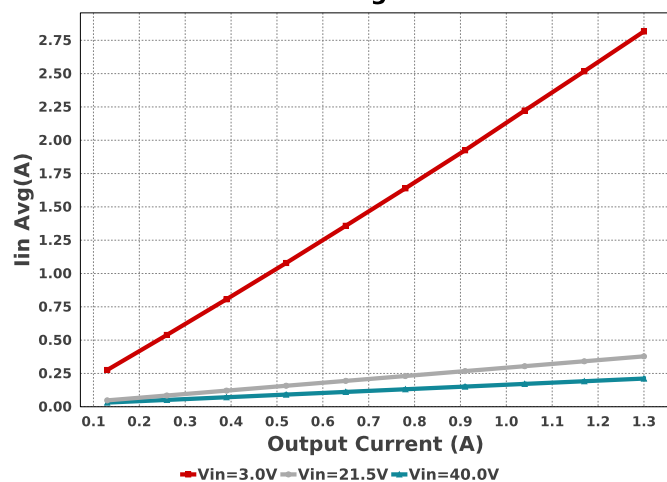


IC Tj

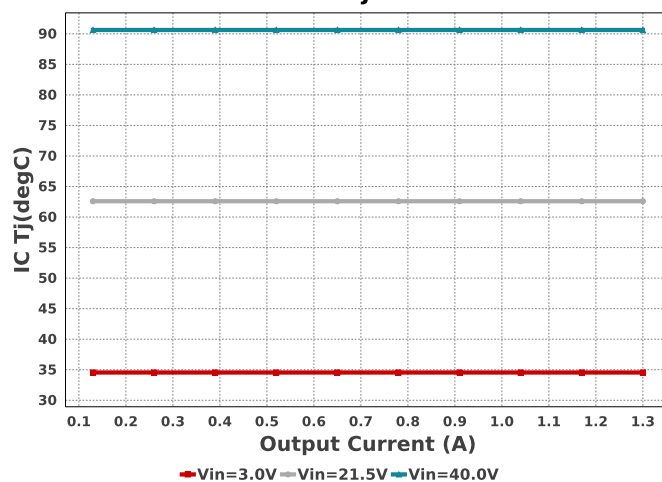


M1 TjOP

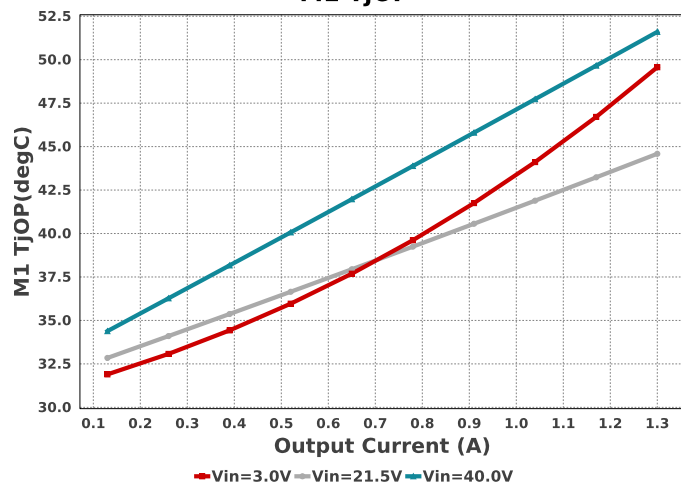


Csep IRMS

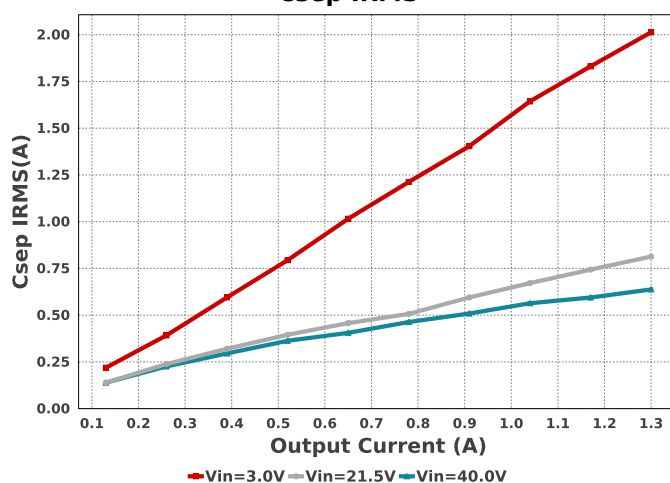


M1 PdCond

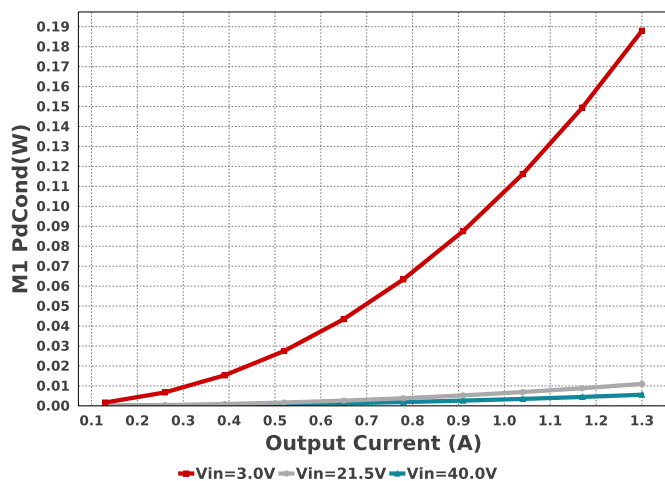


IC Ipk

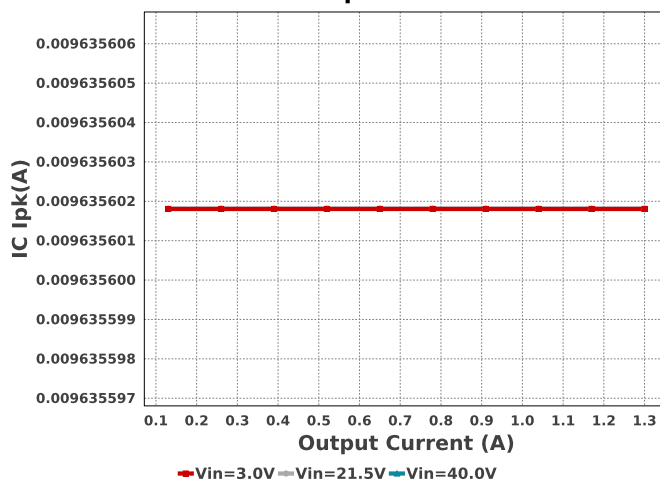


Duty Cycle

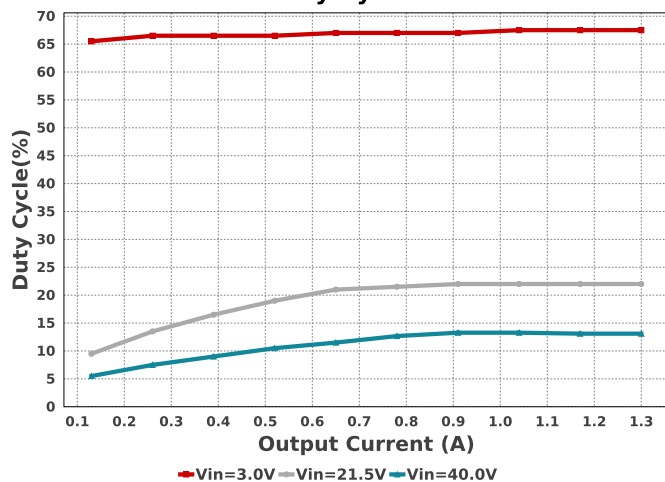


Lout Irms






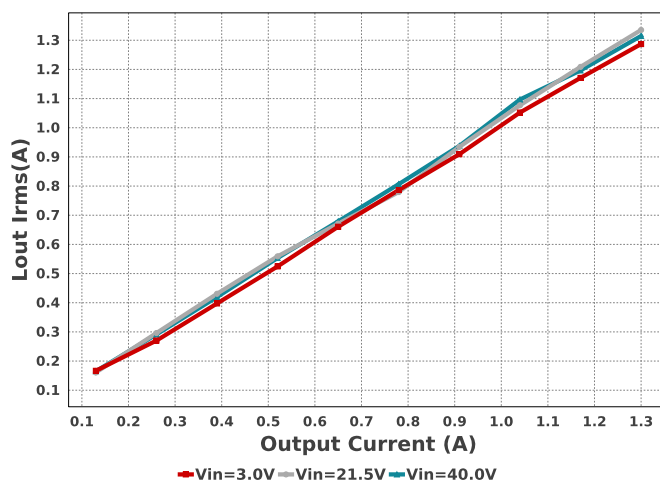








D1 PdCond

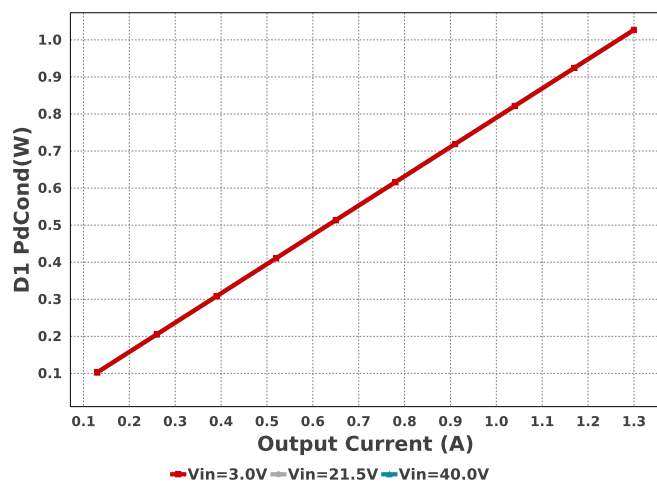


Efficiency

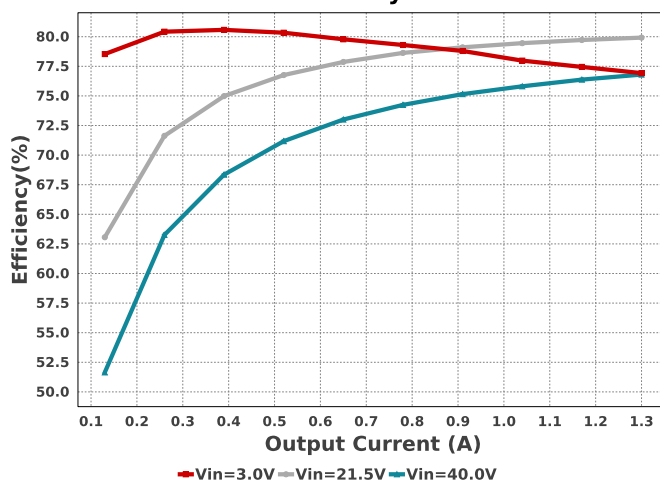

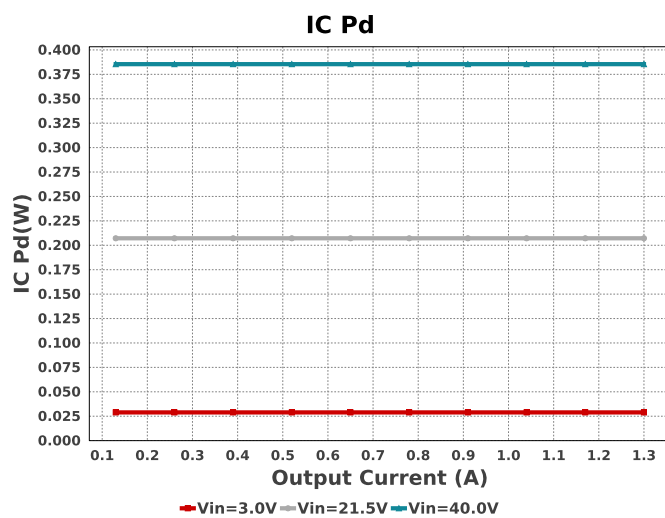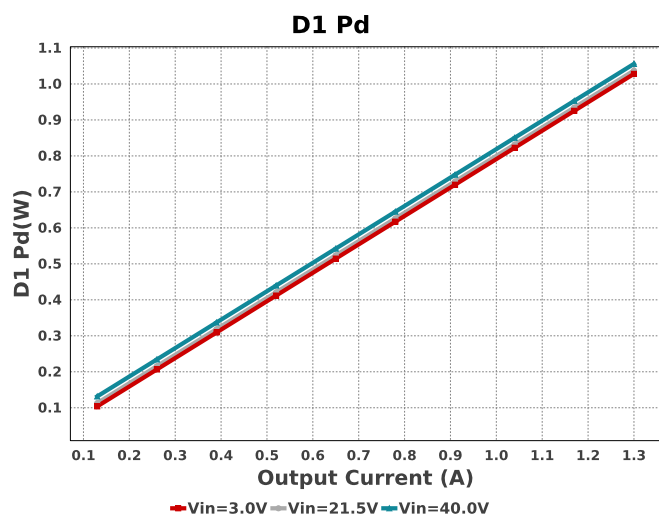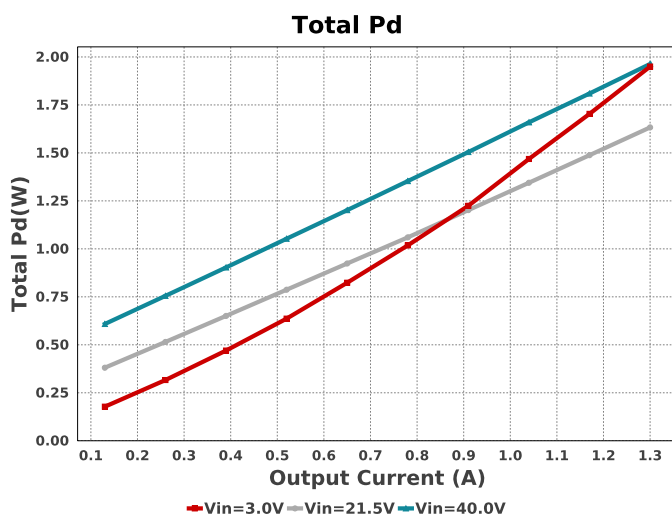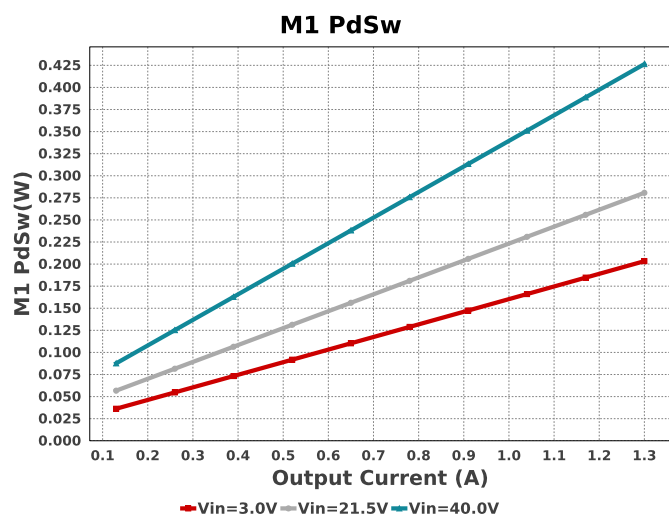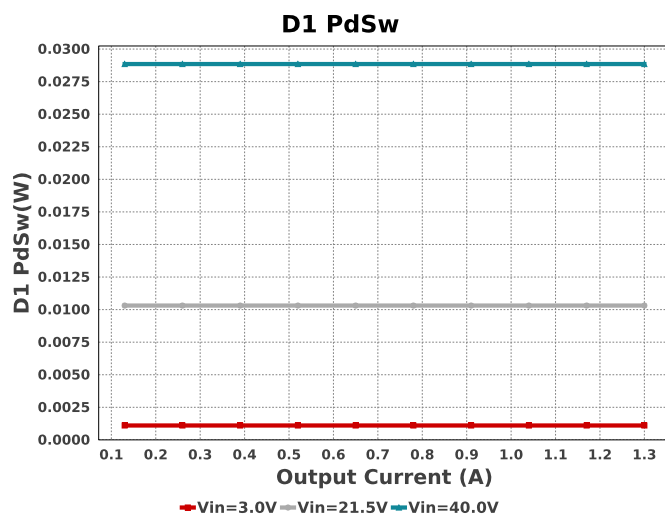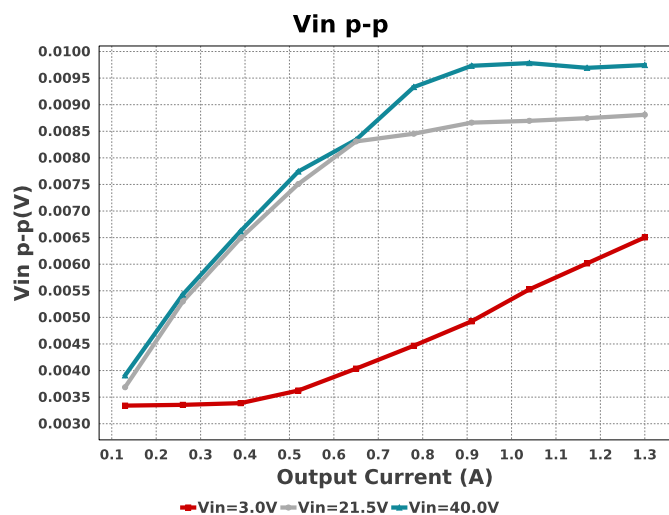

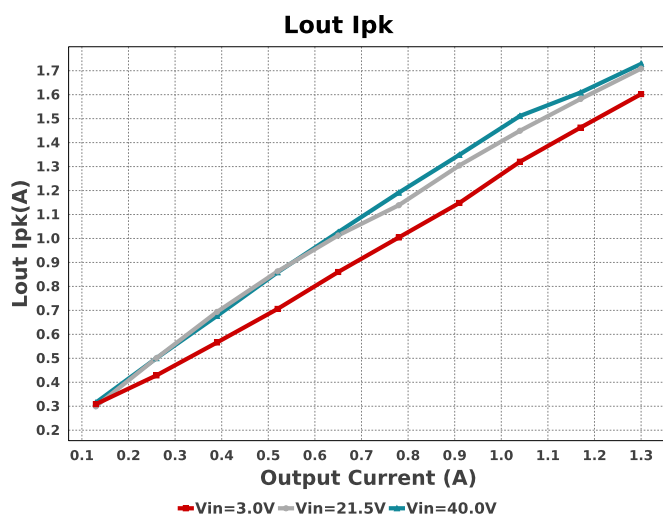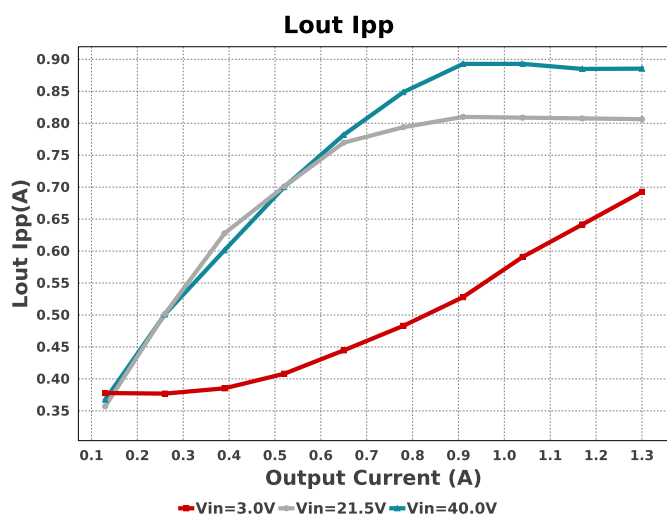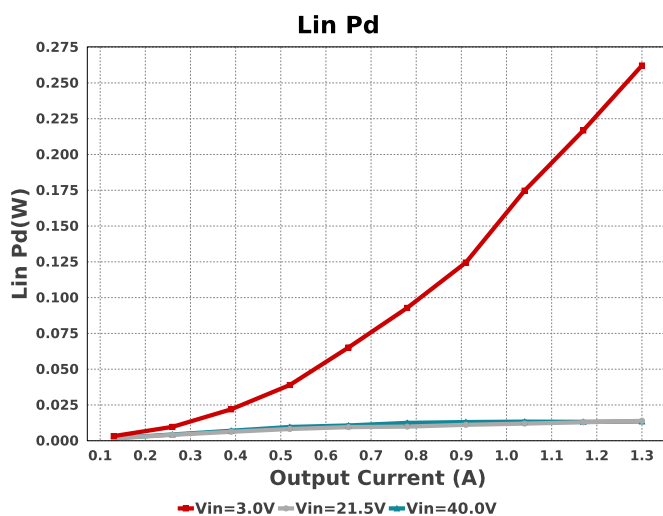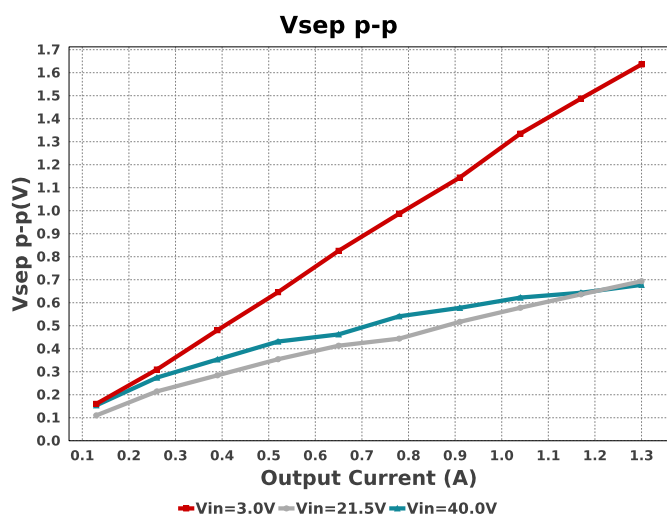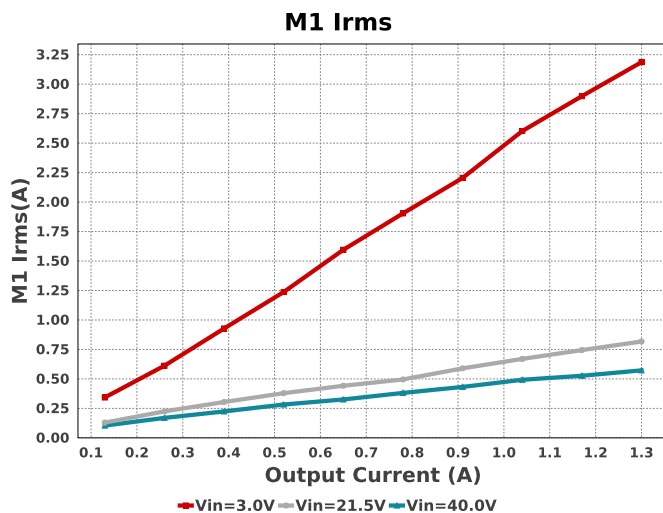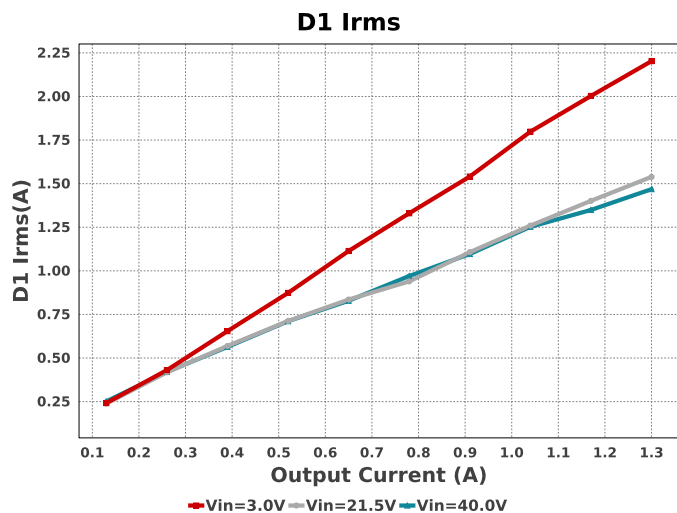

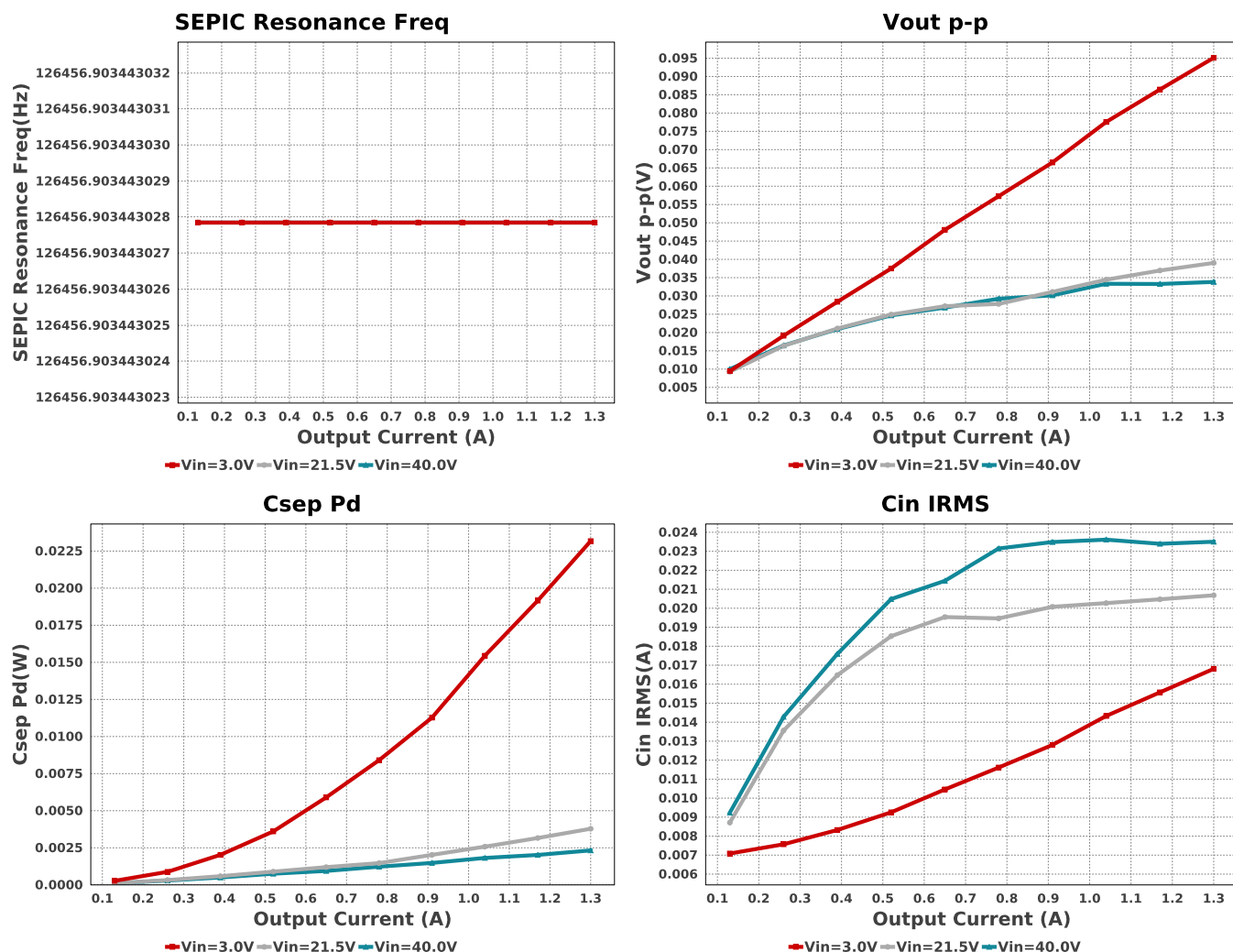

Operating Values

#	Name	Value	Category	Description
1.	Cin IRMS	23.792 mA	Capacitor	Input capacitor RMS ripple current
2.	Cin Pd	67.927 μ W	Capacitor	Input capacitor power dissipation
3.	Cout IRMS	719.743 mA	Capacitor	Output capacitor RMS ripple current
4.	Cout Pd	172.677 μ W	Capacitor	Output capacitor power dissipation
5.	Csep IRMS	638.225 mA	Capacitor	SEPIC capacitor RMS ripple current
6.	Csep Pd	2.329 mW	Capacitor	SEPIC capacitor power dissipation
7.	D1 Irms	1.463 A	Current	D1 Irms
8.	Lin Ipk	702.92 mA	Current	Lin peak current
9.	Lin Irms	391.132 mA	Current	Lin ripple current
10.	Lout Ipk	1.725 A	Current	Lout peak current
11.	Lout Irms	1.308 A	Current	Lout ripple current
12.	D1 Pd	1.056 W	Diode	Diode power dissipation
13.	D1 PdCond	1.027 W	Diode	Diode conduction losses
14.	D1 PdSw	28.566 mW	Diode	Diode switching losses
15.	D1 Tj	74.334 degC	Diode	D1 junction temperature
16.	IC Ipk	9.59 mA	IC	Peak switch current in IC
17.	IC Pd	383.6 mW	IC	IC power dissipation
18.	IC Tj	90.34 degC	IC	IC junction temperature
19.	IC Tolerance	19.0 mV	IC	IC Feedback Tolerance
20.	Iin Avg	211.42 mA	IC	Average input current
21.	SEPIC Resonance Freq	126.457 kHz	IC	SEPIC Resonance Frequency
22.	Vsep p-p	688.053 mV	IC	Peak-to-peak sepic voltage
23.	Lin Ipp	1.052 A	Inductor	Peak-to-peak input inductor ripple current
24.	Lout Ipp	892.031 mA	Inductor	Peak-to-peak output inductor ripple current
25.	M1 Irms	570.522 mA	Mosfet	M1 MOSFET Irms
26.	M1 Pd	427.794 mW	Mosfet	M1 MOSFET total power dissipation
27.	M1 PdCond	5.572 mW	Mosfet	M1 MOSFET conduction losses
28.	M1 PdSw	422.222 mW	Mosfet	M1 MOSFET switching losses
29.	M1 TJOP	51.39 degC	Mosfet	M1 MOSFET junction temperature
30.	IOUT_OP	1.3 A	Op Point	Iout operating point
31.	VIN_OP	40.0 V	Op Point	Vin operating point

#	Name	Value	Category	Description
32.	Lin Pd	13.772 mW	Power	Lin power dissipation
33.	Lout Pd	69.31 mW	Power	Lout power dissipation
34.	Total Pd	1.957 W	Power	Total Power Dissipation
35.	Rsense Pd	2.604 mW	Resistor	LED Current Rsns Power Dissipation
36.	BOM Count	23	System	Total Design BOM count
			Information	
37.	Duty Cycle	13.1 %	System	Duty cycle
			Information	
38.	Efficiency	76.863 %	System	Steady state efficiency
			Information	
39.	FootPrint	545.0 mm ²	System	Total Foot Print Area of BOM components
			Information	
40.	Frequency	270.0 kHz	System	Switching frequency
			Information	
41.	Mode	CCM	System	Conduction Mode
			Information	
42.	Total BOM	NA	System	Total BOM Cost
			Information	
43.	Vin p-p	9.875 mV	System	Peak-to-peak input voltage
			Information	
44.	Vout p-p	33.91 mV	System	Peak-to-peak output ripple voltage
			Information	

Design Inputs

Name	Value	Description
Iout	1.3	Maximum Output Current
VinMax	40.0	Maximum input voltage
VinMin	3.0	Minimum input voltage
Vout	5.0	Output Voltage
base_pn	LM3481	Base Product Number
source	DC	Input Source Type
Ta	30.0	Ambient temperature

WEBENCH® Assembly

Component Testing

Some published data on components in datasheets such as Capacitor ESR and Inductor DC resistance is based on conservative values that will guarantee that the components always exceed the specification. For design purposes it is usually better to work with typical values. Since this data is not always available it is a good practice to measure the Capacitance and ESR values of C_{in} and C_{out} , and the inductance and DC resistance of $L1$ before assembly of the board. Any large discrepancies in values should be electrically simulated in WEBENCH to check for instabilities and thermally simulated in WebTHERM to make sure critical temperatures are not exceeded.

Soldering Component to Board


If board assembly is done in house it is best to tack down one terminal of a component on the board then solder the other terminal. For surface mount parts with large tabs, such as the DPAK, the tab on the back of the package should be pre-tinned with solder, then tacked into place by one of the pins. To solder the tab down to the board place the iron down on the board while resting against the tab, heating both surfaces simultaneously. Apply light pressure to the top of the plastic case until the solder flows around the part and the part is flush with the PCB. If the solder is not flowing around the board you may need a higher wattage iron (generally 25W to 30W is enough).

Initial Startup of Circuit

It is best to initially power up the board by setting the input supply voltage to the lowest operating input voltage 3.0V and set the input supply's current limit to zero. With the input supply off connect up the input supply to V_{in} and GND. Connect a digital volt meter and a load if needed to set the minimum load of the design from V_{out} and GND. Turn on the input supply and slowly turn up the current limit on the input supply. If the voltage starts to rise on the input supply continue increasing the input supply current limit while watching the output voltage. If the current increases on the input supply, but the voltage remains near zero, then there may be a short or a component misplaced on the board. Power down the board and visually inspect for solder bridges and recheck the diode and capacitor polarities. Once the power supply circuit is operational then more extensive testing may include full load testing, transient load and line tests to compare with simulation results.

Load Testing

The setup is the same as the initial startup, except that an additional digital voltmeter is connected between V_{in} and GND, a load is connected between V_{out} and GND and a current meter is connected in series between V_{out} and the load. The load must be able to handle at least rated output power + 50% (7.5 watts for this design). Ideally the load is supplied in the form of a variable load test unit. It can also be done in the form of suitably large power resistors. When using an oscilloscope to measure waveforms on the prototype board, the ground leads of the oscilloscope probes should be as short as possible and the area of the loop formed by the ground lead should be kept to a minimum. This will help reduce ground lead inductance and eliminate EMI noise that is not actually present in the circuit.

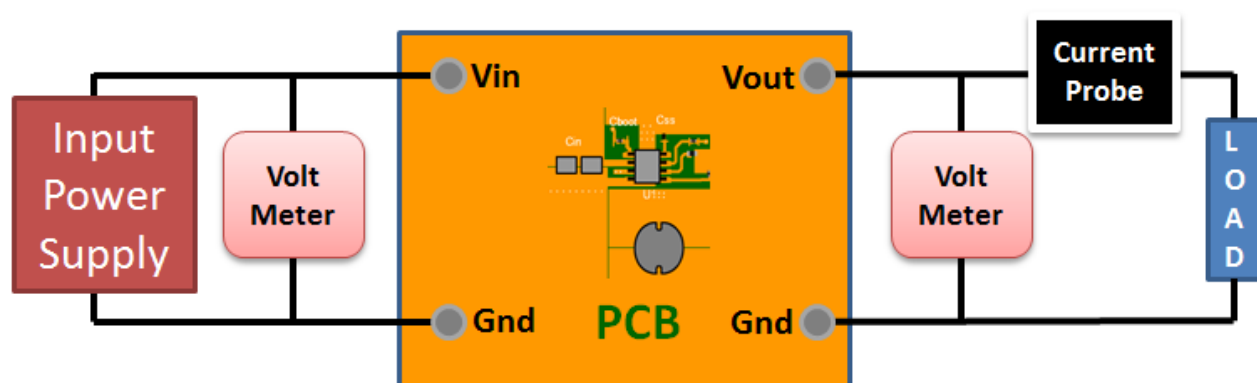

Design Assistance

1. Master key : 08F3F7782B57AA59D562CA9FD0FB323A[v1]
2. **LM3481** Product Folder : <http://www.ti.com/product/LM3481> : contains the data sheet and other resources.

Important Notice and Disclaimer

TI provides technical and reliability data (including datasheets), design resources (including reference designs), application or other design advice, web tools, safety information, and other resources AS IS and with all faults, and disclaims all warranties. These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

Providing these resources does not expand or otherwise alter TI's applicable Terms of Sale or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with TI products.